

Name: _____ Date: _____

Electricity and Circuits

Q1. For each arrangement, find out whether the bulb glows or not.

Ans.



Electricity and Circuits

Q1. For each arrangement, find out whether the bulb glows or not.

Ans.



Circuit is complete. Therefore, bulb will glow.



Circuit is not complete. Therefore, bulb will not glow.



Circuit is open or broken. Therefore, bulb will not glow.



Circuit is not complete. Therefore, bulb will not glow.